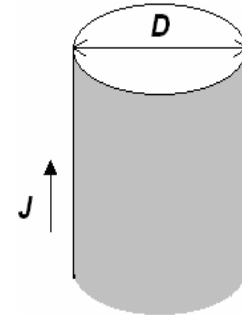





**Q-1)** Figure shows a long conducting wire whose diameter is  $D$ . A current density in the wire is  $J(r) = kr$ , where  $k$  is a constant and  $r$  is the distance from cylindrical axis, parallel to the axis of the wire as shown in Figure. Show that total current in the wire is given by:

$$i = \frac{k\pi D^3}{12}$$




**Q-2)** The isolated two conductors A and B having equal length of 10m and a common radii of 2mm are connected in series to another conductor C having length of 5m and radius of 4mm as seen in figure. The resistivities of the conductors are  $1.6 \times 10^6$ ,  $1.6 \times 10^6$  and  $3.2 \times 10^6 \Omega\text{-m}$ , respectively. If a potential difference 40 volt is applied between the ends of the composite wire determine:

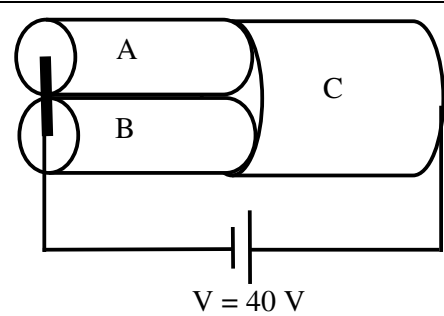


- the resistance value of each wire,
- the current density in each wire,
- the potential differences across each wire.

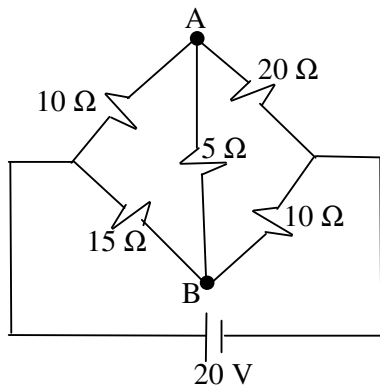**Q-3)** Determine the voltage across the resistor connected between the points A and B for the circuit given below.



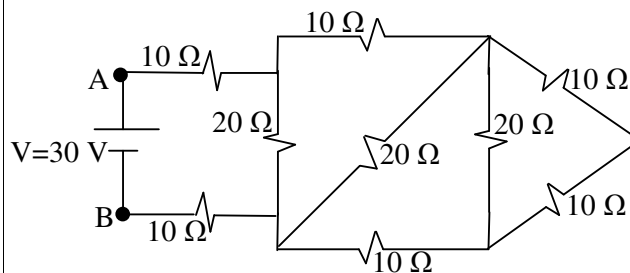**Q-4)**

- What is the equivalent resistance between the points A and B in the circuit given below?
- What is the current through the equivalent resistance?



**Q-5)** An RC circuit is discharged by closing a switch at time  $t=0$ . The initial potential difference across the capacitor is 100 V. If the potential difference has decreased to 10 Volt after 10 s, if  $C=0.05 \mu\text{F}$ .

- What is the time constant of the circuit?
- What will the potential difference across the capacitor after  $t=12$  sec?
- What will the amount of charge be on each plate of the capacitor after  $t=12$  sec?
- What is the current through the resistor after  $t=12$  sec?

